

Course Code: CS223

Course Name: Digital Design

Section: 1

Project


Mustafa Mert Gülhan

22201895

Date: 05.05.2024

Detailed Description of UART Design:

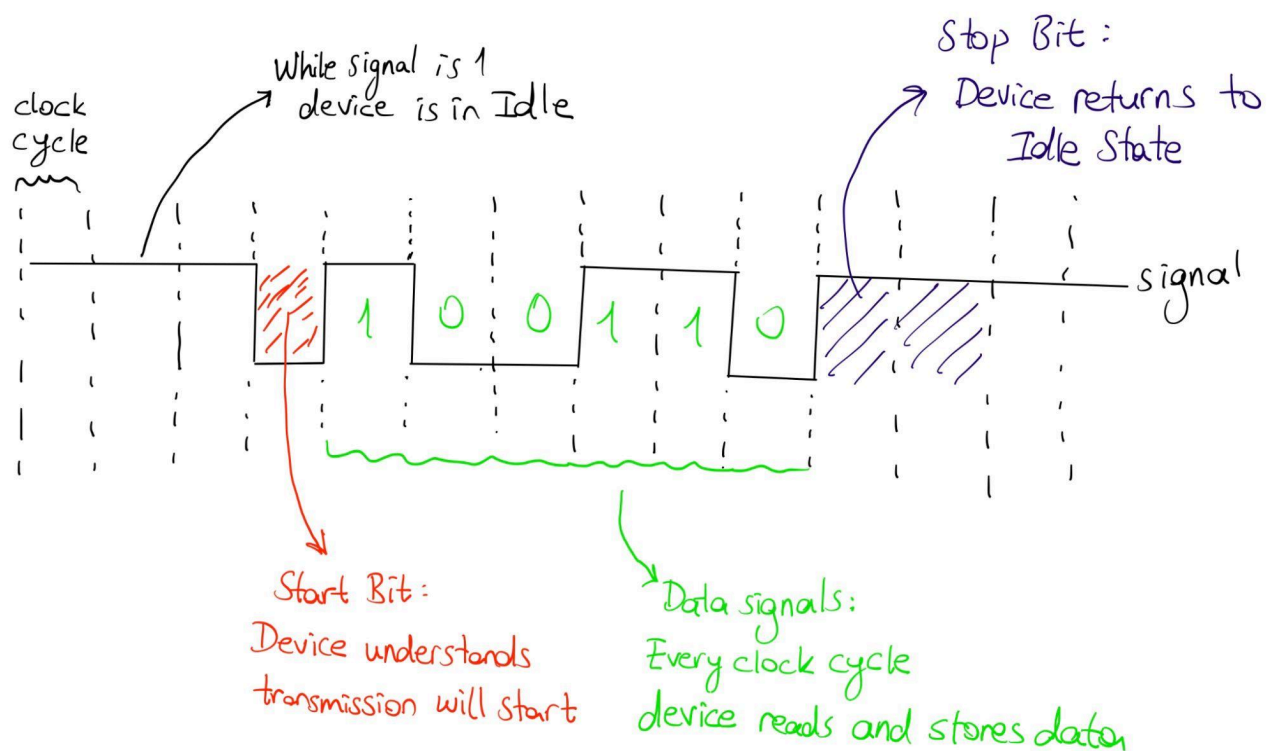
Mainly the idea behind the UART device is to send multiple bits of data to another UART device with a single signal in a way that it can read the data from that signal and store it. The signal works in this way



The UART_tx is responsible for generating this signal where UART_rx is responsible for reading that signal and storing the data. To work properly both tx and rx devices must agree on the amount of bits will be transmitted and the clock cycle.


State Diagram for UART_tx:

 Inputs: in (8 bit), en (bit) Local Storage: $bitpos$ (3 bit)
Output: out (bit)




State Diagram for UART_rx:

Inputs: in (bit),
Output: out (8 bit)

 


State Diagram for Display:

 


$\text{Out} = \text{buf}[\hat{\text{index}}]$


State Diagram for Continuous Transfer

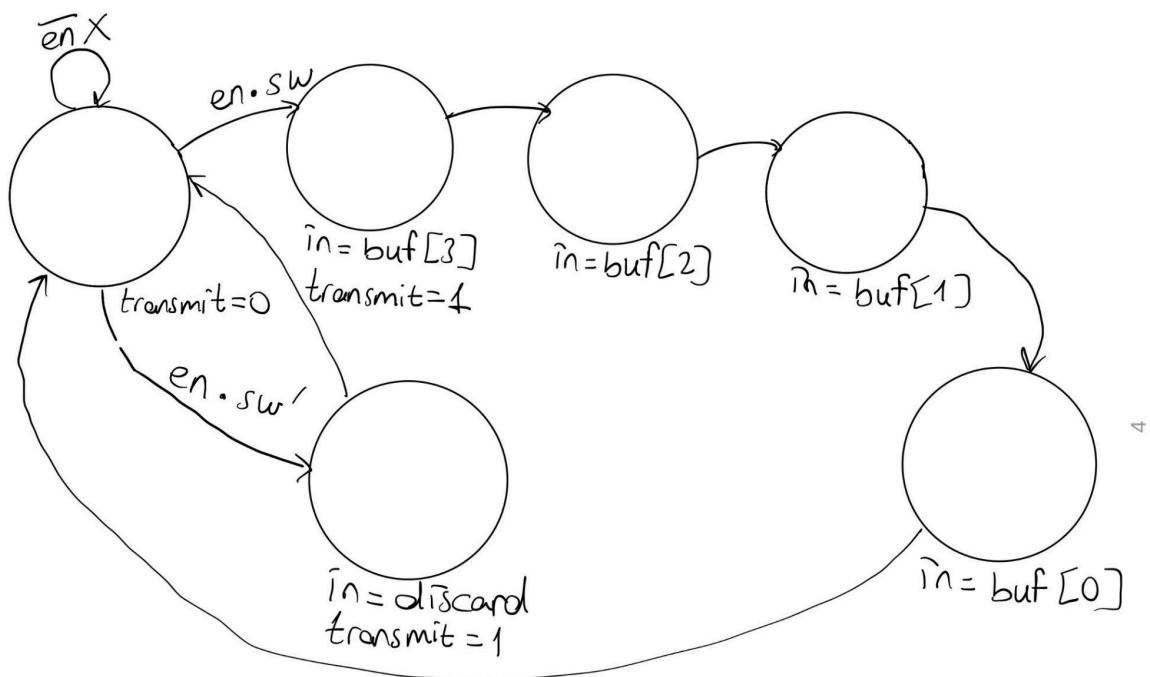


Schematic for UART tx:

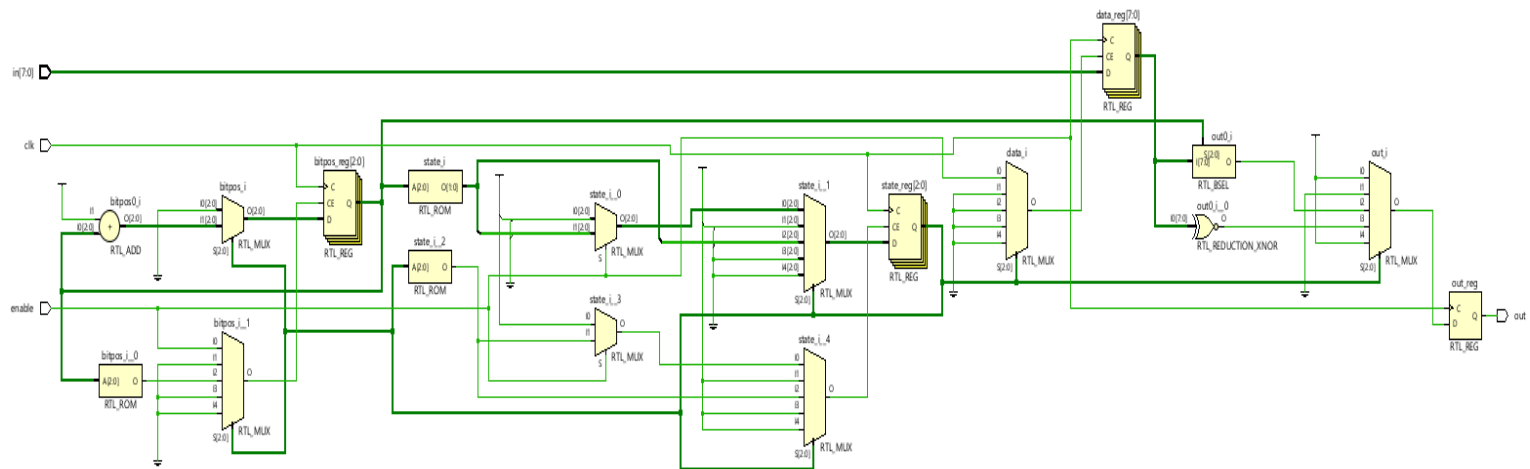


Schematic for UART rx:

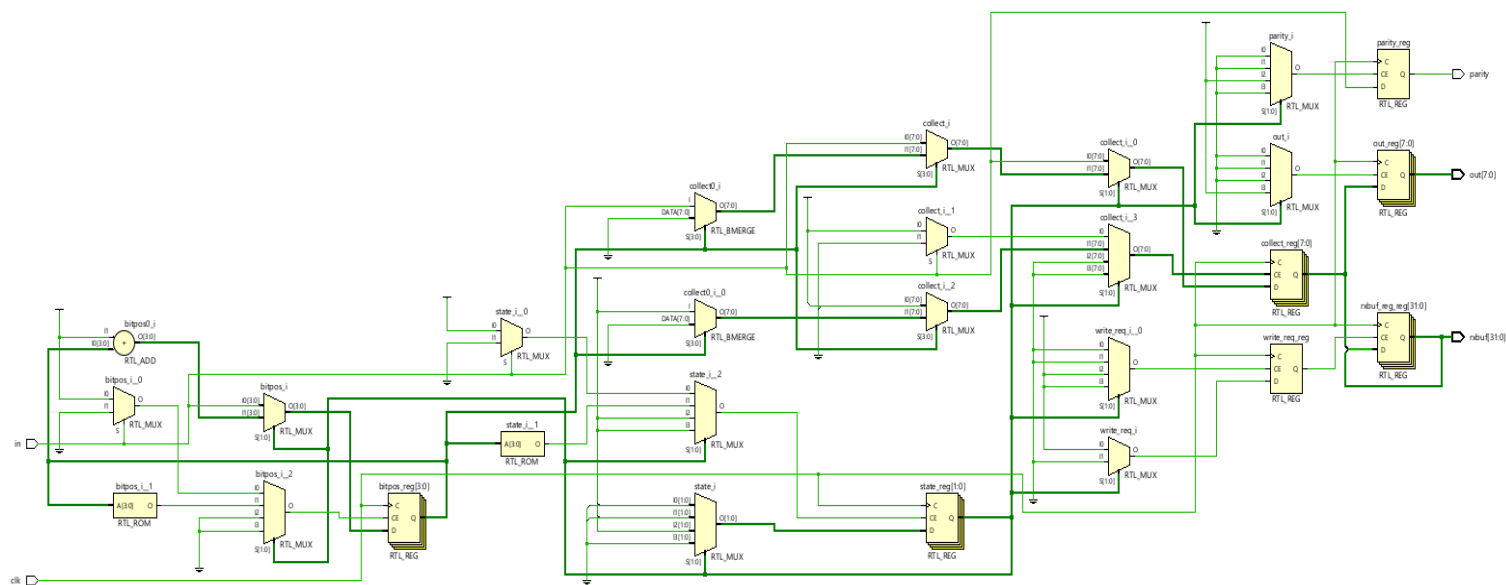


Schematic for Memory Arrays

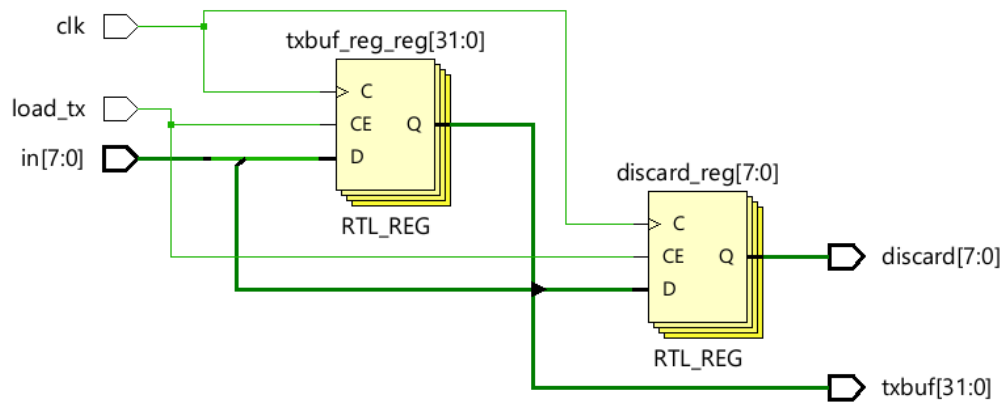

Schematic for 7-Segment Display:

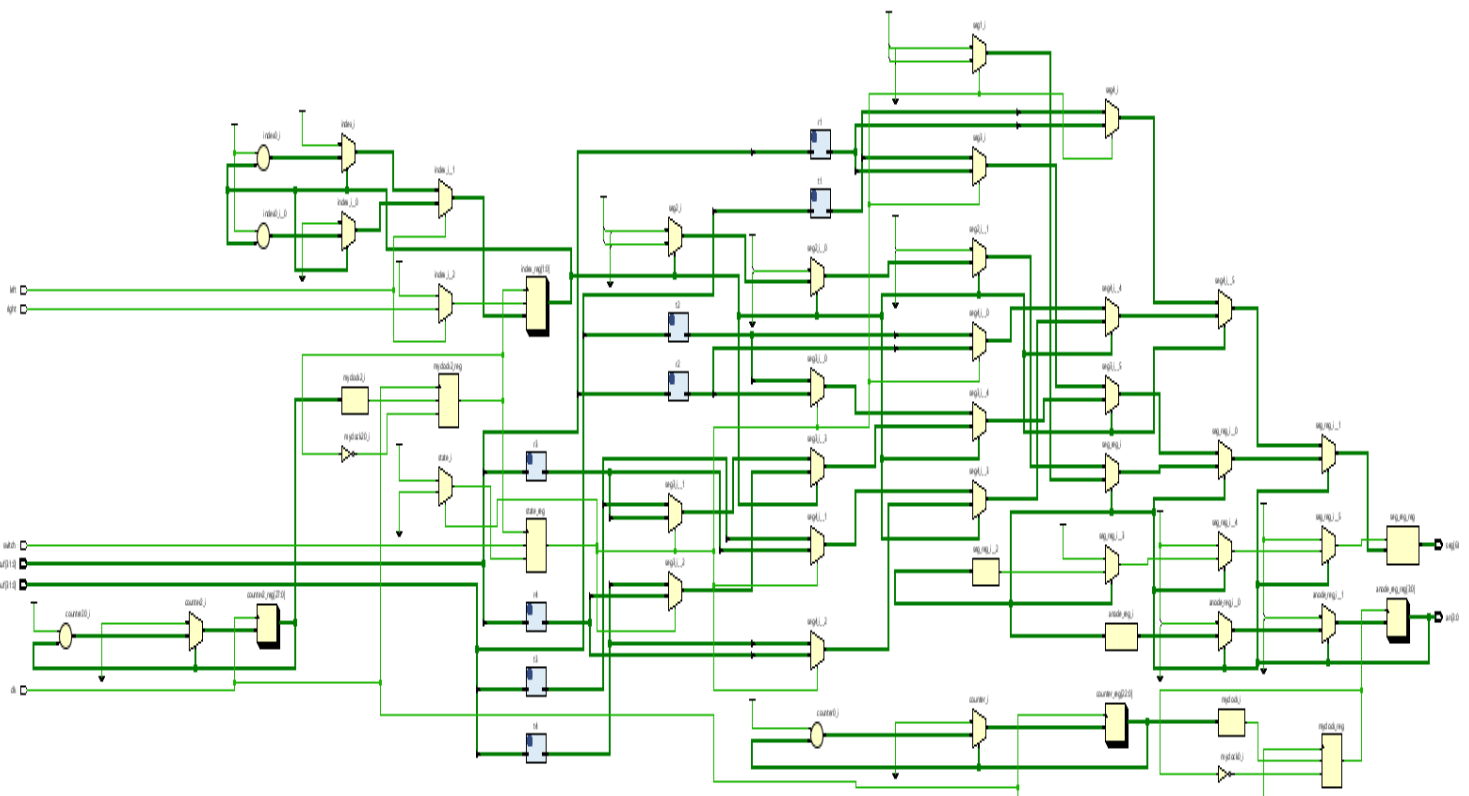

Schematic for Continuous Transfer:

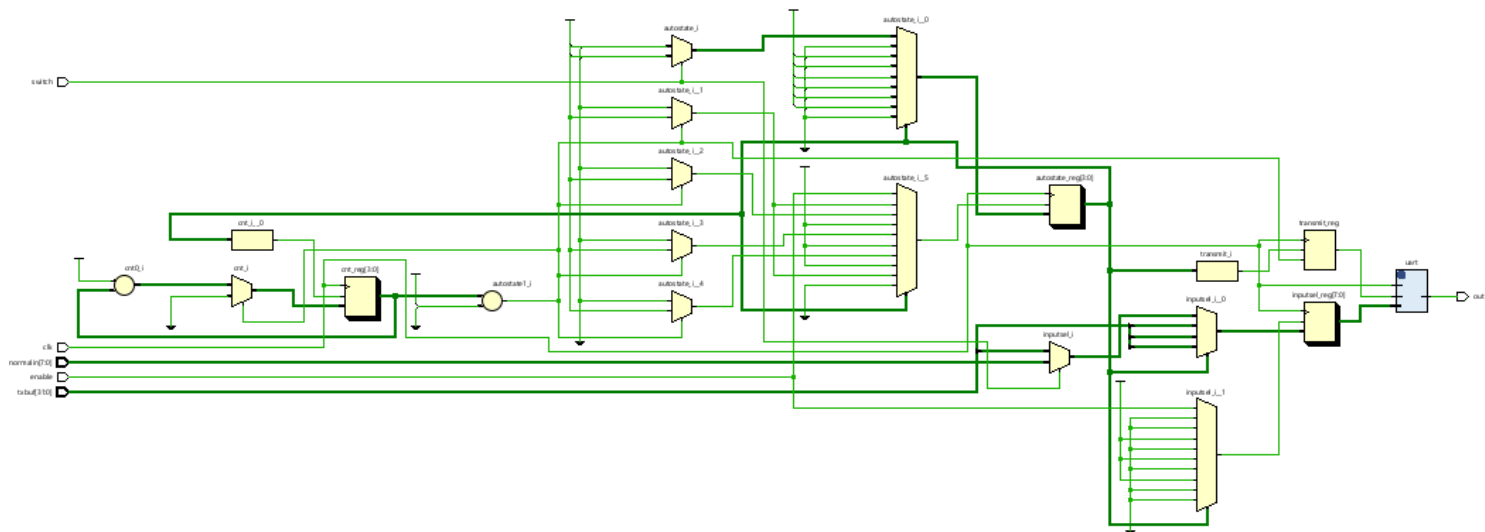

Testbenches:

```
module autotransfer_tb();
    logic [31:0]txbuf;
    logic clk = 0;
    logic en = 0;
    logic out;
    logic [7:0] currout;
    logic par;
    logic [31:0] rxbuf;
    logic switchin = 0;
    logic [7:0] normalin;

    autotransfer dut(txbuf,clk,en,switchin,normalin,out);
    uart_rx test(out,clk,currout,par,rxbuf);

    always begin
        clk = ~clk; #5;
    end
end
```

```

        initial begin
            txbuf = 32'b10010001_01101100_11110010_00011101;
normalin = 8'b00010001; switchin = 1; #20;
            en = 1; #20; en = 0; #630;
            switchin = 0; #20; en = 1; #20; en = 0;
        end

```

```

endmodule

```

```

module uart_rx_tb();
    logic [7:0] tx_in;
    logic clk = 1;
    logic en;
    logic tx_out;
    logic [7:0] out;
    logic parity;
    logic [31:0] rxbuf;

    uart_tx signal(tx_in,clk,en,tx_out);
    uart_rx dut(tx_out,clk,out,parity,rxbuf);
    always begin
        clk = ~clk; #5;
    end
end

```

```

    initial begin

```

```

        en = 1; tx_in = 8'b10010011; #20; en = 0; #100;
        en = 1; tx_in = 8'b11000010; #20; en = 0; #100;
        en = 1; tx_in = 8'b10010101; #20; en = 0; #100;
        en = 1; tx_in = 8'b11110011; #20; en = 0; #100;
        en = 1; tx_in = 8'b10110111; #20; en = 0; #100;

```

```

    end
endmodule

```

```

module buttonlatch_tb();

```



```

    logic clk= 0;
    logic btn,stable;

    always begin
        clk = ~clk; #10;
    end
    buttonlatch dut(clk,btn,stable);
    initial begin
        btn = 0; #20;
        btn = 1; #50;
        btn = 0; #50;
        btn = 1; #50;
        btn = 0;
    end
endmodule

```

```

module sevenseg_tb();
    logic [7:0] in;
    logic [13:0] out;
    sevenseg dut(in,out);
    initial begin
        in = 8'b1001_0111; #20;
        in = 8'b1111_1000; #20;
        in = 8'b1011_0011; #20;
    end
endmodule

```

```

module uart_tx_tb();
    logic [7:0]in;
    logic clk = 1;
    logic out;

    uart_tx dut(0,0,in,clk,1'b1,out);
    always begin
        clk = ~clk; #10;
    end
    initial begin

```

```

        in = 8'b10110110; #205;
        in = 8'b01110001;
    end
endmodule

```

Appendix

```

module sevenseg(input logic [7:0] in, output logic [13:0]
out );
    always @(*) begin
        case(in[3:0])
            4'b0000: out[6:0] = 7'b0000001;
            4'b0001: out[6:0] = 7'b1001111;
            4'b0010: out[6:0] = 7'b0010010;
            4'b0011: out[6:0] = 7'b0000110;
            4'b0100: out[6:0] = 7'b1001100;
            4'b0101: out[6:0] = 7'b0100100;
            4'b0110: out[6:0] = 7'b0100000;
            4'b0111: out[6:0] = 7'b0001111;
            4'b1000: out[6:0] = 7'b0000000;
            4'b1001: out[6:0] = 7'b0000100;
            4'b1010: out[6:0] = 7'b0001000; //a
            4'b1011: out[6:0] = 7'b1100000; //b
            4'b1100: out[6:0] = 7'b1110010; //c
            4'b1101: out[6:0] = 7'b1000010; //d
            4'b1110: out[6:0] = 7'b0110000; //e
            4'b1111: out[6:0] = 7'b0111000; //f
            default: out[6:0] = 7'b1111110;
        endcase
        case(in[7:4])
            4'b0000: out[13:7] = 7'b0000001;
            4'b0001: out[13:7] = 7'b1001111;
            4'b0010: out[13:7] = 7'b0010010;
            4'b0011: out[13:7] = 7'b0000110;

```

```

4'b0100: out[13:7] = 7'b1001100;
4'b0101: out[13:7] = 7'b0100100;
4'b0110: out[13:7] = 7'b0100000;
4'b0111: out[13:7] = 7'b0001111;
4'b1000: out[13:7] = 7'b0000000;
4'b1001: out[13:7] = 7'b0000100;
4'b1010: out[13:7] = 7'b0001000; //a
4'b1011: out[13:7] = 7'b1100000; //b
4'b1100: out[13:7] = 7'b1110010; //c
4'b1101: out[13:7] = 7'b1000010; //d
4'b1110: out[13:7] = 7'b0110000; //e
4'b1111: out[13:7] = 7'b0111000; //f
default: out[13:7] = 7'b1111110;

```

```

    endcase

```

```

end

```

```

endmodule

```

```

module display(
input logic [31:0]txbuf,
input logic [31:0]rxbuf,
input logic switch,
input logic right,
input logic left,
input logic clk,
output logic[3:0] an,
output logic [6:0] seg);

```

```

    logic[13:0] tx0;
    logic[13:0] tx1;
    logic[13:0] tx2;
    logic[13:0] tx3;

```

```

    logic[13:0] rx0;
    logic[13:0] rx1;
    logic[13:0] rx2;
    logic[13:0] rx3;

```

```

sevensseg t1(txbuf[7:0],tx0);
sevensseg t2(txbuf[15:8],tx1);
sevensseg t3(txbuf[23:16],tx2);
sevensseg t4(txbuf[31:24],tx3);

sevensseg r1(rxbuf[7:0],rx0);
sevensseg r2(rxbuf[15:8],rx1);
sevensseg r3(rxbuf[23:16],rx2);
sevensseg r4(rxbuf[31:24],rx3);

parameter state_tx = 0;
parameter state_rx = 1;
reg state = state_tx;

reg [6:0]seg_reg = 7'b1110000;
reg [3:0]anode_reg = 4'b0111;

logic [6:0] seg1 = 7'b1110000; //displays t or x on
current state
logic [6:0] seg2 = 7'b0000001; //display the index
logic [6:0] seg3 = 0;
logic [6:0] seg4 = 0;

logic[22:0] counter = 0;
logic[27:0] counter2 = 0;
logic myclock = 0;
logic myclock2 = 0;

logic [1:0] index = 0;

always @(posedge myclock2) begin
    if(switch) begin
        if(state == state_tx)
            state = state_rx;
        else

```

```

        state = state_tx;
    end
end

always @(posedge myclock2) begin
    if(right) begin
        if(index == 2'b11)
            index <= 0;
        else
            index <= index + 1'b1;
        end
    end
    if(left) begin
        if(index == 2'b00)
            index <= 2'b11;
        else
            index <= index - 1'b1;
        end
    end
end

always @(state) begin
    if(state == state_tx)
        seg1 <= 7'b1110000;
    else
        seg1 <= 7'b1111010;
    end
end

always @(index) begin
    if(index == 2'b00) begin
        seg2 <= 7'b0000001;
        if(state == state_tx) begin
            seg3 <= tx0[13:7];
            seg4 <= tx0[6:0];
        end
    end
    else begin
        seg3 <= rx0[13:7];
        seg4 <= rx0[6:0];
    end
end

end
else if(index == 2'b01) begin

```

```

        seg2 <= 7'b1001111;
        if(state == state_tx) begin
            seg3 <= tx1[13:7];
            seg4 <= tx1[6:0];
        end
        else begin
            seg3 <= rx1[13:7];
            seg4 <= rx1[6:0];
        end
    end
end
else if(index == 2'b10) begin
    seg2 <= 7'b0010010;
    if(state == state_tx) begin
        seg3 <= tx2[13:7];
        seg4 <= tx2[6:0];
    end
    else begin
        seg3 <= rx2[13:7];
        seg4 <= rx2[6:0];
    end
end
end
else begin
    seg2 <= 7'b0000110;
    if(state == state_tx) begin
        seg3 <= tx3[13:7];
        seg4 <= tx3[6:0];
    end
    else begin
        seg3 <= rx3[13:7];
        seg4 <= rx3[6:0];
    end
end
end
end
always @(posedge clk) begin
    if(counter == 100000)
        begin
            counter <= 0;
        end
end

```

```

        myclock <= ~myclock;
    end
    else
    begin
        counter <= counter+1;
    end
end

always @(posedge clk) begin
    if(counter2 == 100000000)
    begin
        counter2 <= 0;
        myclock2 <= ~myclock2;
    end
    else
    begin
        counter2 <= counter2+1;
    end
end

always @(posedge myclock) begin //myclock to clk on
testbench
    if(anode_reg == 4'b1110)
        anode_reg <= 4'b1101;
    else if(anode_reg == 4'b1101)
        anode_reg <= 4'b1011;
    else if(anode_reg == 4'b1011)
        anode_reg <= 4'b0111;
    else
        anode_reg <= 4'b1110;
end

always @(anode_reg) begin
    if(anode_reg == 4'b1110)
        seg_reg <= seg4;
    else if(anode_reg == 4'b1101)
        seg_reg <= seg3;

```

```

        else if(anode_reg == 4'b1011)
            seg_reg <= seg2;
        else if(anode_reg == 4'b0111)
            seg_reg <= seg1;
    end

    assign an = anode_reg;
    assign seg = seg_reg;
endmodule

module uart_rx
(
    input logic in,
    input logic clk,
    output logic [7:0] out,
    output logic parity,
    output logic [31:0] rxbuf
);

    initial begin
        out = 8'b0;
    end

    parameter STATE_START = 2'b00;
    parameter STATE_DATA = 2'b01;
    parameter STATE_PARITY= 2'b10;
    parameter STATE_STOP = 2'b11;

    reg [1:0] state = STATE_START;
    reg [3:0] bitpos = 4'd0;
    reg [7:0] collect = 8'b0;
    reg [31:0] rxbuf_reg = 32'b0;

    reg write_req = 0; // New register for write request

    logic [7:0] discard = 0;

```



```

always @(posedge clk) begin
    case(state)

        STATE_START: begin
            if(!in) begin
                state <= STATE_DATA;
                bitpos <= 4'd0;
                collect <= 0;
            end
        end
    end
    STATE_DATA: begin
        if(bitpos == 4'd7) begin
            collect[bitpos] <= in;
            state <= STATE_PARITY;
        end
        else begin
            collect[bitpos] <= in; //bitpos[2:0] if
not work
            bitpos <= bitpos + 1'b1;
        end
    end
    STATE_PARITY: begin
        state <= STATE_STOP;
        parity <= in;
        write_req <= 1'b1;
    end
    STATE_STOP: begin
        write_req <= 1'b0;
        out <= collect;
        state <= STATE_START;
    end
    default: begin
        state <= STATE_START;
    end
endcase
end

```

```

always @(posedge clk) begin
    if (write_req) begin
        rxbuf_reg[31:8] <= rxbuf_reg[23:0];
        rxbuf_reg[7:0] <= collect;
    end
end

assign rxbuf = rxbuf_reg; //en yeni [7:0] en eski
[31:24]

endmodule

module autotransfer(
    input logic [31:0] txbuf,
    input logic clk,
    input logic enable,
    input logic switch,
    input logic [7:0] normalin,
    output logic out
);
    parameter ASTATE_IDLE = 4'b0000;
    parameter ASTATE_TX4 = 4'b0001;
    parameter ASTATE_LOADTX3 = 4'b0010;
    parameter ASTATE_TX3 = 4'b0011;
    parameter ASTATE_LOADTX2 = 4'b0100;
    parameter ASTATE_TX2 = 4'b0101;
    parameter ASTATE_LOADTX1 = 4'b0110;
    parameter ASTATE_TX1 = 4'b0111;
    parameter ASTATE_NORMAL = 4'b1000;

    logic [7:0] inputsel;
    logic[3:0] autostate = ASTATE_IDLE;
    logic transmit = 0;

    logic [3:0]cnt = 0;

```

```

uart_tx uart(inputsel,clk,transmit,out);

always @(posedge clk) begin
    case(autostate)
    ASTATE_IDLE: begin
        if(enable) begin
            if(switch) begin
                autostate <= ASTATE_TX4;
                inputsel <= txbuf[31:24];
            end
            else begin
                autostate <= ASTATE_NORMAL;
                inputsel <= normalin;
            end
        end
    end
    ASTATE_NORMAL: begin
        transmit <= 1;
        if(cnt != 4'b1010) begin
            cnt <= cnt + 1;
        end
        else begin
            autostate <= ASTATE_IDLE;
            cnt <= 0;
            transmit <= 0;
        end
    end
    ASTATE_TX4: begin
        transmit <= 1;
        if(cnt != 4'b1010) begin
            cnt <= cnt + 1;
        end
        else begin
            autostate <= ASTATE_LOADTX3;
            cnt <= 0;
            transmit <= 0;
        end
    end
end

```

```

        end
    end
    ASTATE_LOADTX3: begin
        inputsel <= txbuf[23:16];
        autostate <= ASTATE_TX3;
    end
    ASTATE_TX3: begin
        transmit <= 1;
        if(cnt != 4'b1010) begin
            cnt <= cnt + 1;
        end
        else begin
            autostate <= ASTATE_LOADTX2;
            cnt <= 0;
            transmit <= 0;
        end
    end
end
    ASTATE_LOADTX2: begin
        inputsel <= txbuf[15:8];
        autostate <= ASTATE_TX2;
    end
    ASTATE_TX2: begin
        transmit <= 1;
        if(cnt != 4'b1010) begin
            cnt <= cnt + 1;
        end
        else begin
            autostate <= ASTATE_LOADTX1;
            cnt <= 0;
            transmit <= 0;
        end
    end
end
    ASTATE_LOADTX1: begin
        inputsel <= txbuf[7:0];
        autostate <= ASTATE_TX1;
    end
    ASTATE_TX1: begin

```

```

        transmit <= 1;
        if(cnt != 4'b1010) begin
            cnt <= cnt + 1;
        end
        else begin
            autostate <= ASTATE_IDLE;
            cnt <= 0;
            transmit <= 0;
        end
    end
endcase
end
endmodule

```

```

module uart_tx
(
    input logic [7:0]in,
    input logic clk,
    input logic enable,
    output logic out
);
    initial begin
        out = 1'b1;
    end
    parameter STATE_IDLE = 3'b000;
    parameter STATE_START = 3'b001;
    parameter STATE_DATA = 3'b010;
    parameter STATE_PARITY = 3'b011;
    parameter STATE_STOP = 3'b100;

    reg [7:0] data = 8'b0;
    reg [2:0] bitpos = 3'b0;
    reg [2:0] state = STATE_IDLE;
    reg [31:0] txbuf_reg = 0;

```

```

always @(posedge clk) begin
    case(state)
        STATE_IDLE: begin
            out <= 1'b1;
            if(enable) begin
                state <= STATE_START;
                data <= in;
                bitpos <= 3'b0;
            end
        end
        STATE_START: begin
            out <= 1'b0;
            state <= STATE_DATA;
        end
        STATE_DATA: begin
            if(bitpos == 3'd7) begin
                state = STATE_PARITY;
            end
            else begin
                bitpos <= bitpos + 3'd1;
            end
            out <= data[bitpos];
        end
        STATE_PARITY: begin
            out <= ~^data;
            state <= STATE_IDLE;
        end
        default: begin
            out <= 1'b1;
            state <= STATE_IDLE;
        end
    endcase
end
endmodule

module buttonlatch(input logic clk,btn, output logic
stable);

```

```

    initial begin
        stable = 0;
    end
    reg isclicked = 0;
    reg temp = 0;
    always @(posedge clk) begin
        if(isclicked && btn) begin
            stable <= 0;
            isclicked <= 0;
        end
        if(!isclicked && btn && !temp) begin
            stable <= 1;
            temp <= 1;
            isclicked <= 1;
        end
        if(!isclicked && !btn) begin
            temp <= 0;
        end
    end

end
endmodule

module txbuf(input logic clk,input logic load_tx, input
logic[7:0] in, output logic[31:0]txbuf, output logic
[7:0] discard);
    reg [31:0]txbuf_reg = 0;
    initial begin
        discard = 0;
    end
    always @(posedge clk) begin
        if(load_tx) begin
            discard <= txbuf_reg[31:24];
            txbuf_reg[31:24] <= txbuf_reg[23:16];
            txbuf_reg[23:16] <= txbuf_reg[15:8];
            txbuf_reg[15:8] <= txbuf_reg[7:0];
            txbuf_reg[7:0] <= in;
        end
    end
end

```

```

    end

    assign txbuf = txbuf_reg;

endmodule

module baudclk(input logic clk, output logic baudclk);
    parameter baudcount = 100_000_000 / 115200;
    parameter baudcount_width = $clog2(baudcount);
    reg [baudcount_width-1:0] clk_acc = 0;

    assign baudclk = (clk_acc == 10'd0);

    always @(posedge clk) begin
        if (clk_acc == baudcount[baudcount_width-1:0])
            clk_acc <= 0;
        else
            clk_acc <= clk_acc + 10'b1;
        end
    end

endmodule

module uart(
    input logic [7:0]switchin,
    input logic transmit4,
    input logic clk,
    input logic switch,
    input logic left,
    input logic right,
    input logic tx_write,
    input logic tx_enable,
    input logic sw15,

    output logic [7:0] txbufled,
    output logic [7:0] rxbufled,
    output logic [3:0] an,
    output logic [6:0] seg

```



```

);
    //clk generator with specified baudrate
    logic tx_out; //output logic tx_out yapılacak
    logic rx_in; //input logic rx_in yapılacak


    logic baudclk;
    logic tx_out_reg;
    logic [31:0] txbuf;
    logic [31:0] rxbuf;
    logic [7:0] rx_out;
    logic parity;
    logic stable_enable;
    logic stable_write;
    baudclk clkgen(clk,baudclk);


    //module for handling 4byte txbuf read,write
    logic [7:0] discard;


    buttonlatch bt2(baudclk,tx_write,stable_write);
    txbuf
txbufwriter(baudclk,stable_write,switchin,txbuf,discard);


    //uart modules
    buttonlatch bt(baudclk,tx_enable,stable_enable);
    //uart_tx
tx(switchin,baudclk,stable_enable,tx_out_reg);
    autotransfer
at_tx(txbuf,baudclk,stable_enable,sw15,switchin,tx_out_re
g); //switchin to discard
    uart_rx rx(tx_out_reg,baudclk,rx_out,parity,rxbuf);
//tx_out_reg to rx_in
    display(txbuf,rxbuf,switch,right,left,clk,an,seg);


    assign txbufled = txbuf[7:0];
    assign rxbufled = rxbuf[31:24];
    assign tx_out = tx_out_reg;

```

endmodule