

**Course Code: CS223**

**Course Name: Digital Design**

**Section: 1**


**Lab 3**

**Mustafa Mert Gülhan**


**22201895**

**Date: 17.03.2024**
 
## Graphical Symbol and Truth Table for 2:1 Mux



## Logic Diagram for 2:1 Mux

 


## Behavioral 2:1 Multiplexer Module

```
module twomux_behavioral(input logic s,d0,d1,
output logic y);
    assign y = (d0 & (~s)) | (d1 & s);
endmodule
```

### **Behavioral 2:1 Multiplexer Testbench**

```
module twomux_behavioral_tb();
    logic d0,d1,s,y;
    twomux_behavioral dut(s,d0,d1,y);
    initial begin
        s=0; d0=0; d1=0; #20;
        s=0; d0=0; d1=1; #20;
        s=0; d0=1; d1=0; #20;
        s=0; d0=1; d1=1; #20;
        s=1; d0=0; d1=0; #20;
        s=1; d0=0; d1=1; #20;
        s=1; d0=1; d1=0; #20;
        s=1; d0=1; d1=1; #20;
    end
endmodule
```
 
### **Graphical Symbol and Truth Table for 4:1 Mux**



### **Behavioral 4:1 Multiplexer Module**

```
module fourmux_behavioral(input logic
s[1:0],i[3:0], output logic y);
    logic w1,w2;
    twomux_behavioral mux1(s[0],i[0],i[1],w1);
    twomux_behavioral mux2(s[0],i[2],i[3],w2);
    twomux_behavioral mux3(s[1],w1,w2,y);
endmodule
```

### **Behavioral 4:1 Multiplexer Testbench**

```
module fourmux_behavioral_tb();
    logic s[1:0],i[3:0],y;
    fourmux_behavioral dut(s,i,y);
    initial begin
```


```

        s={0,0}; i={0,0,0,0}; #20;
s={0,0}; i={1,0,0,0}; #20;
        s={0,0}; i={0,1,0,0}; #20;
        s={0,0}; i={0,0,1,0}; #20;
        s={0,0}; i={1,1,1,0}; #20;
        s={0,0}; i={0,0,0,1}; #20;
        s={0,1}; i={0,0,0,0}; #20;
        s={0,1}; i={1,1,0,1}; #20;
        s={0,1}; i={0,0,1,0}; #20;
        s={1,0}; i={0,0,0,0}; #20;
        s={1,0}; i={1,0,1,1}; #20;
        s={1,0}; i={0,1,0,0}; #20;
        s={1,1}; i={0,0,0,0}; #20;
        s={1,1}; i={0,1,1,1}; #20;
        s={1,1}; i={1,0,0,0}; #20;

    end
endmodule


```

 **Implementation of Function f using 4:1 mux**




- Description: Basically, acts as a 4 to 1 multiplexer with selects  $w_1$  as  $s_1$ ,  $w_2$  as  $s_0$  and  $w_3$  as input0, input3 and  $w_3'$  for input1, input2
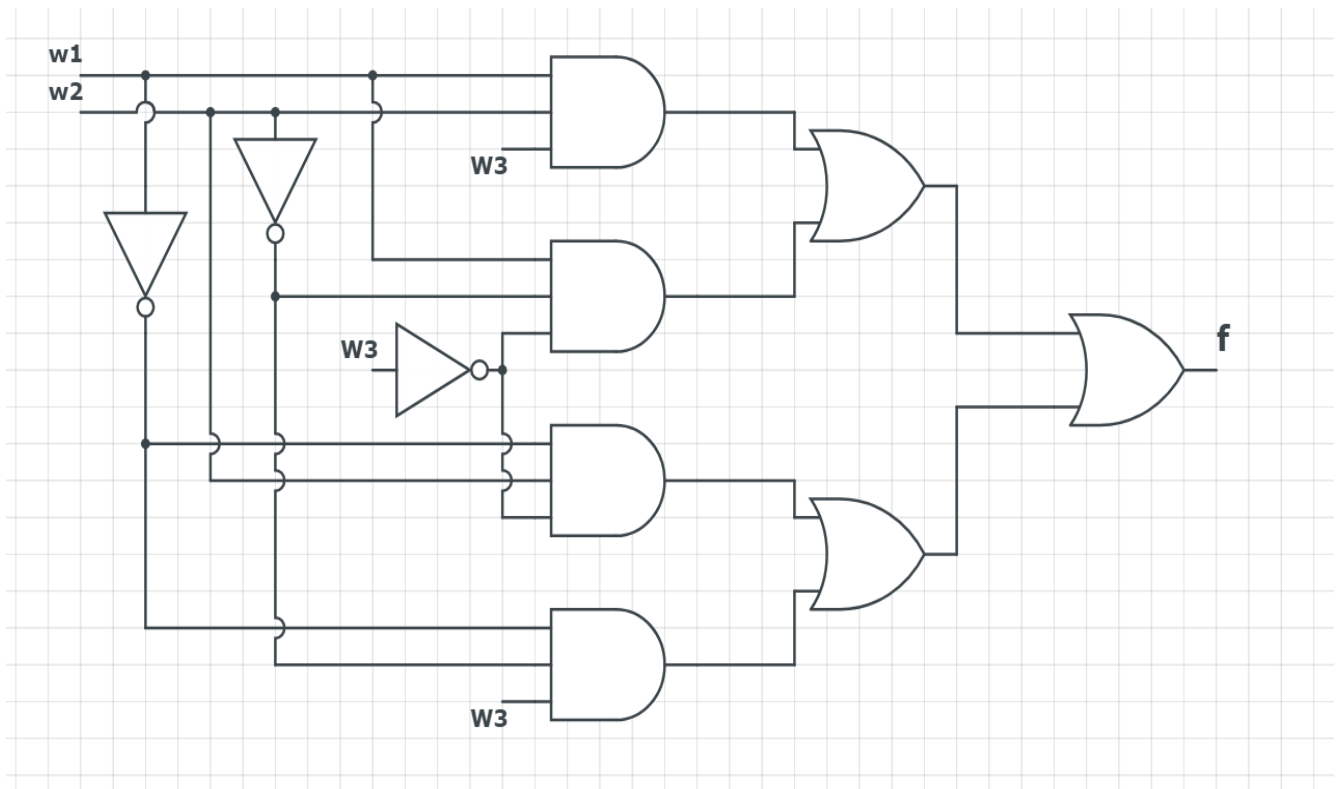
### Logic Diagram of Function $f$ using 4:1 mux



 
### Implementation of Function $f$ using 2:1 mux



- Description: Similar to 4:1 version because 4:1 mux can be implemented by using three 2:1 multiplexers.
 
### Logic Diagram of Function f using 2:1 mux




### Operation of Function f

The operation realized is 3 input XOR gate


### Implementation of Function g



 

- Description: input0 and input3 are always constant. However, input1 and input2 depend on  $w_3$  while  $w_1$  and  $w_2$  act as select. Basically, if more than 1 input is true output is true.

 
### Logic Diagram of Function $g$ using 4:1 Mux



**Modified Truth Table for Function g**


$w_1$	$w_2$	$w_3$	$g$
0	0	X	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	X	1
 
## Implementation of Function g using 2:1 Mux



- Description: Similar to 4 to 1 Mux version however only  $w_1$  acts as a select in this version.
 
## Logic Diagram of Function g using 2:1 Mux



**Modified Truth Table of Function g**

$w_1$	$w_2$	$w_3$	$g$
0	0	X	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	X	1

### **Behavioral Module of Function g using 2:1 Mux**


```
module functiong_behavioral(input logic
w1,w2,w3, output logic g);
    logic mid1,mid2;
    assign mid1 = (w2&w3)&(~w1);
    assign mid2 = (w2|w3)&w1;
    assign g = mid1 | mid2;
endmodule
```

### **Behavioral Module Testbench of Function g**

```
module functiong_behavioral_tb();
    logic w1,w2,w3,g;
    functiong_behavioral dut(w1,w2,w3,g);
    initial begin
        w1=0;w2=0;w3=0; #20;
        w1=0;w2=0;w3=1; #20;
        w1=0;w2=1;w3=0; #20;
        w1=0;w2=1;w3=1; #20;
        w1=1;w2=0;w3=0; #20;
        w1=1;w2=0;w3=1; #20;
        w1=1;w2=1;w3=0; #20;
```

```
w1=1;w2=1;w3=1; #20;  
end  
endmodule
```


### Graphical Symbol of 2 to 4 Decoder

 

### Truth Table of 2 to 4 Decoder

Enable	Inputs		Outputs			
E	A <sub>1</sub>	A <sub>0</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

### Logic Diagram of 2 to 4 Decoder

 

### Behavioral Module of 2 to 4 Decoder

```

module fourdecoder_behavioral(input logic
a[1:0],e, output logic y[3:0]);
    assign y[3] = a[1] & a[0] & e;
    assign y[2] = a[1] & (~a[0]) & e;
    assign y[1] = (~a[1]) & a[0] & e;
    assign y[0] = (~a[1]) & (~a[0]) & e;
endmodule

```

### **Behavioral Testbench of 2 to 4 Decoder**

```

module fourdecoder_behavioral_tb();
    logic a[1:0],e,y[3:0];
    fourdecoder_behavioral
dut(a[1:0],e,y[3:0]);
    initial begin
        a={0,0}; e=1; #20;
        a={0,1}; e=1; #20;
        a={1,0}; e=1; #20;
        a={1,1}; e=1; #20;
        a={0,0}; e=0; #20;
        a={0,1}; e=0; #20;
        a={1,0}; e=0; #20;
    end
endmodule

```



```


        a={1,1}; e=0; #20;

    end

endmodule

```

### Logic Diagram of 3 to 8 Decoder

 

### Structural 3 to 8 Decoder Module

```

module eightdecoder_structural(input logic a[2:0],e,
output logic y[7:0]);

```

```

    logic en1,en2,af2;
    not(af2,a[2]);
    and(en1,af2,e);
    and(en2,a[2],e);
    fourdecoder_behavioral first(a[1:0],en1,y[3:0]);
    fourdecoder_behavioral second(a[1:0],en2,y[7:4]);
endmodule

```

### **Structural 3 to 8 Decoder Testbench Module**


```

module eightdecoder_structural_tb();
    logic a[2:0],e,y[7:0];
    eightdecoder_structural
dut(a[2:0],e,y[7:0]);
    initial begin
        a={0,0,0}; e=1; #20;
        a={0,0,1}; e=1; #20;
        a={0,1,0}; e=1; #20;
        a={0,1,1}; e=1; #20;
        a={1,0,0}; e=1; #20;
        a={1,0,1}; e=1; #20;
        a={1,1,0}; e=1; #20;
        a={1,1,1}; e=1; #20;
    end
endmodule

```

```
a={0,0,0}; e=0; #20;  
a={0,0,1}; e=0; #20;  
a={0,1,0}; e=0; #20;  
a={0,1,1}; e=0; #20;  
a={1,0,0}; e=0; #20;  
a={1,0,1}; e=0; #20;  
a={1,1,0}; e=0; #20;  
a={1,1,1}; e=0; #20;  
end  
endmodule
```

### **Block Diagram of 8 to 1 Mux**

 

### Module of 8 to 1 Mux

```

module eightmux(input logic i[7:0],s[2:0],
output logic y);
    logic w1,w2;

```

```

    fourmux_behavioral m1(s[1:0],i[3:0],w1);
    fourmux_behavioral m2(s[1:0],i[7:4],w2);
    assign y = (~(s[2]) & w1) | (s[2] & w2);
endmodule

```

### **Testbench Module of 8 to 1 Mux**

```

module eightmux_tb();
    logic i[7:0],s[2:0],y;
    eightmux dut(i[7:0],s[2:0],y);
    initial begin
        i = {0,0,0,0,0,0,0,0}; s = {0,0,0}; #20;
        i = {0,0,0,0,0,0,0,1}; s = {0,0,0}; #20;
        i = {0,0,0,0,0,0,0,0}; s = {0,0,1}; #20;
        i = {0,0,0,0,0,0,1,0}; s = {0,0,1}; #20;
        i = {0,0,0,0,0,0,0,0}; s = {0,1,0}; #20;
        i = {0,0,0,0,0,1,0,0}; s = {0,1,0}; #20;
        i = {0,0,0,0,0,0,0,0}; s = {0,1,1}; #20;
        i = {0,0,0,0,1,0,0,0}; s = {0,1,1}; #20;
        i = {0,0,0,0,0,0,0,0}; s = {1,0,0}; #20;
        i = {0,0,0,1,0,0,0,0}; s = {1,0,0}; #20;
        i = {0,0,0,0,0,0,0,0}; s = {1,0,1}; #20;
    end
endmodule


```

```

i = {0,0,1,0,0,0,0,0}; s = {1,0,1}; #20;
i = {0,0,0,0,0,0,0,0}; s = {1,1,0}; #20;
i = {0,1,0,0,0,0,0,0}; s = {1,1,0}; #20;
i = {0,0,0,0,0,0,0,0}; s = {1,1,1}; #20;
i = {1,0,0,0,0,0,0,0}; s = {1,1,1}; #20;
end
endmodule

```
 
### Block Diagram of Function F(A,B,C,D,E)



### SystemVerilog Module of Function F(A,B,C,D,E)

```
module functionF(input logic a,b,c,d,e, output
logic f);
    logic
    decin[1:0],decout[3:0],muxin[7:0],muxsel[2:0];
    assign decin = {b,a};
    fourdecoder_behavioral
    decoder(decin,1,decout);
    assign muxin =
    {decout[2],~b,1,decout[2],0,a,decout[3],decout[
    0]};
    assign muxsel = {e,d,c};
    eightmux mux(muxin,muxsel,f);
endmodule
```